

Exp no: 4

Title :

Date:

Series and Parallel

12-11-2021

Connection

Aim:


To study the properties of series and parallel connection.

Apparatus:


LT spice software tool

Circuit Diagram:

Series Circuit:

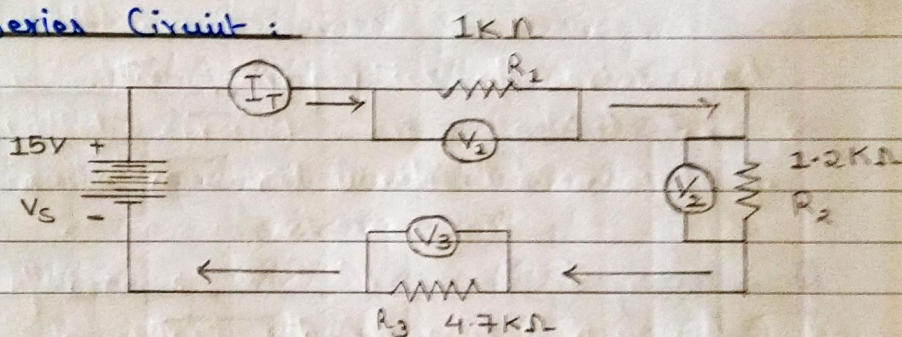

Parallel Circuit:

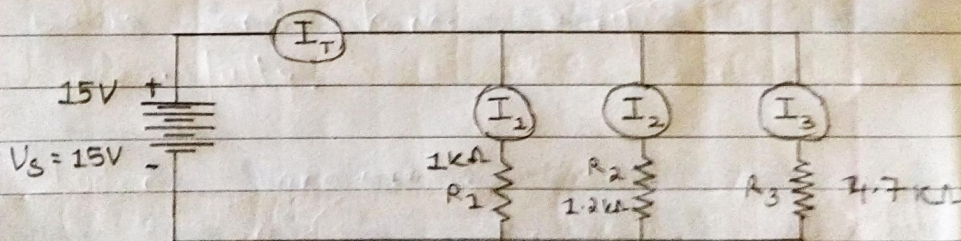

Procedure:

- 1) Draw the series and parallel circuits in the LT spice schematic.



- 2) Apply the voltage and resistance values.
- 3) Label the nodes at appropriate places in the circuit.
- 4) Go to Simulate tab and select edit simulation command.
- 5) Select operating point analysis in the edit simulation command.
- 6) Run the simulation.
- 7) Calculate the potential difference across each resistor and check for  $V_s = V_1 + V_2 + V_3$ .
- 8) Calculate the current through each resistor and check for  $I_r = I_1 + I_2 + I_3$ .

### Theoretical Calculations:

Calculate the current through each resistor and check for  $I_r = I_1 + I_2 + I_3$ .

$$I(R_1) = 0.015$$

$$I(R_2) = 0.0125$$

$$I(R_3) = 0.0039449$$

$$I_r = 0.03069445$$

for  $V_s = V_1 + V_2 + V_3$



$$V(R_1) = 2.1739$$

$$V(R_2) = 2.6087$$

$$V(R_3) = 10.2174$$

$$V_{\text{Total}} = 15.149961 \approx 15$$

Comparison of theoretical values to the simulated values:

	Theoretical values	Simulated values
$V_s$ (Volt)	15	15
$I_T$ (mA)	0.030915	0.0306925

Result:

The properties of series and parallel circuits are studied through simulation and verified successfully.

Inference:

The theoretical value is the same as the same as the simulated value and hence verified successfully.

Student Signature:

S.P. Ashwath

(Name: Ashwath Suresh Babu Piriya)