

Exp no: 5	Title:
Date: 12-11-2021	Half wave rectifier and full wave rectifier

Aim:


- 1) To Setup a half wave rectifier and to find the dc value of rectified voltage.
- 2) To set up a full wave rectifier and to find the dc value of rectified voltage.

Apparatus:


LT spice software tool

Circuit Diagram:


Half wave Rectifier

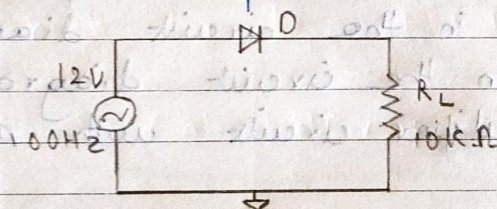

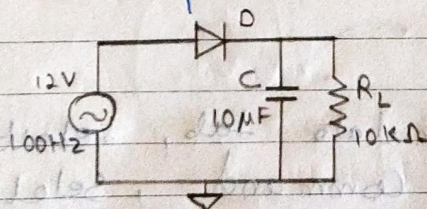
Half wave rectifier with capacitor filter



Full wave rectifier

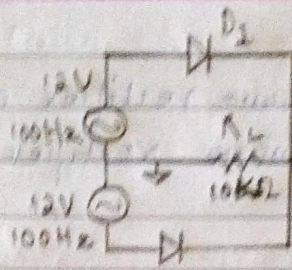

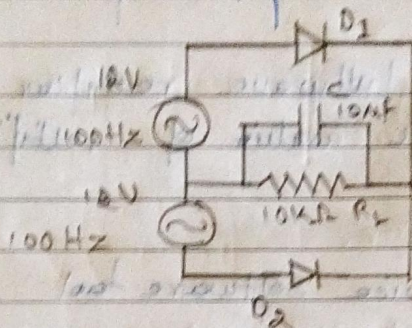Full wave rectifier with capacitor filter




Procedure :

- 1) Draw the circuit in LT spice schematic as shown in the circuit diagram as shown in the circuit diagram for each rectifier circuit with and without filters.
- 2) Apply values to all the elements in the circuit.
- 3) Go to Simulate tab, select tab edit simulation command, select transient analysis since we have to observe the waveforms with respect to time.
- 4) Select the stop time according to the

frequency of input waveform.

- 5) Run the simulation
- 6) Observe the input and output waveforms
- 7) Calculate the V_m value by attaching the cursor to output waveform.
- 8) Calculate the V_{dc} , V_{rms} , ripple factor for Half wave and full wave rectifier.

Model Graph:

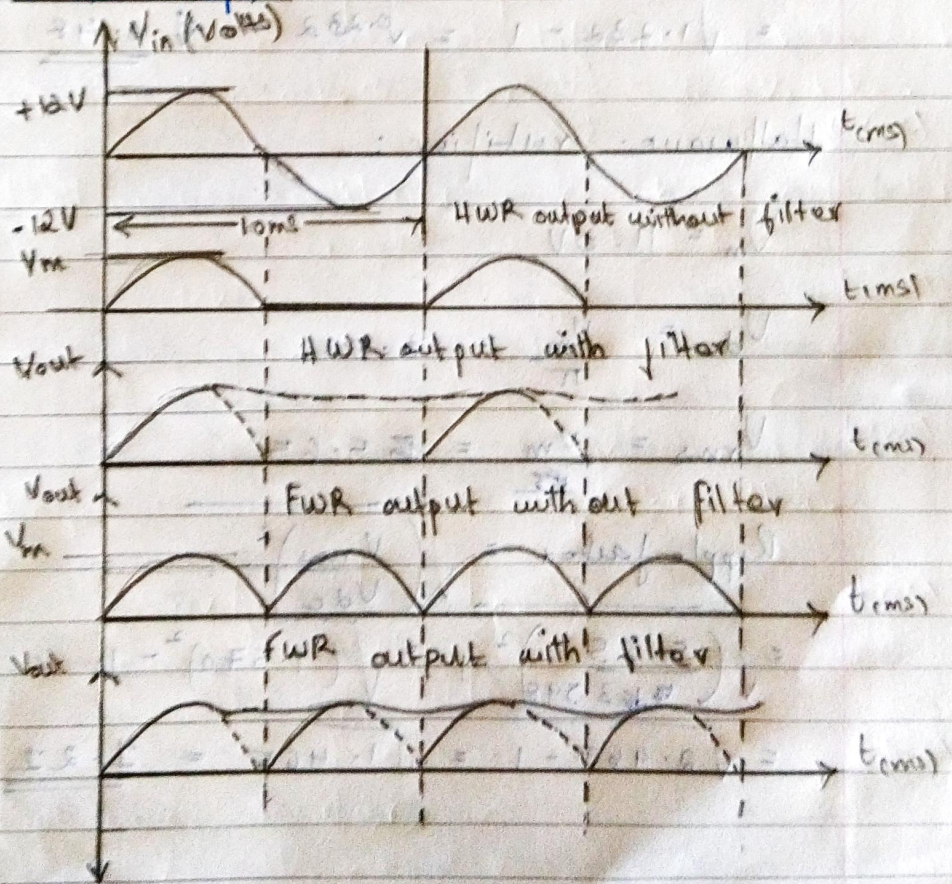

Calculations:

Full wave rectifier:

$$V_m = 11.3 \text{ V}$$

$$V_{dc} = \frac{2V_m}{\pi} = \frac{2(11.3)}{3.14} = 7.197$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{11.3}{\sqrt{2}} = 7.990$$

$$\text{Ripple factor} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

$$= \sqrt{\left(\frac{7.990}{7.197}\right)^2 - 1} = \sqrt{(1.110)^2 - 1}$$

$$= \sqrt{1.232 - 1} = \sqrt{0.232} = \underline{\underline{0.48}}$$

Half wave rectifier:

$$V_m = 11.3 \text{ V}$$

$$V_{dc} = \frac{V_m}{\pi} = 3.598$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 5.65$$

$$\text{Ripple factor} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

$$= \sqrt{\left(\frac{5.65}{3.598}\right)^2 - 1} = \sqrt{(1.570)^2 - 1}$$

$$= \sqrt{2.465 - 1} = \sqrt{1.465} = \underline{\underline{1.21}}$$

Comparison of theoretical with simulated values :

Ripple factor	Theoretical Value	Simulated value
HWR	1.21	1.21
FWR	0.48	0.48

Result :

The half wave and full wave rectified outputs are simulated successfully

inferences :

- 1) the theoretical value of ripple factor for half-wave rectifier is same as simulated value.
- 2) The theoretical value of ripple factor for full wave rectifier is same as simulated value.
- 3) The amplitude of the rectified output is reduced when the capacitor is connected to the resistor. Hence the ripple factor can be reduced.

Inference :

The theoretical value of r is the same as the simulated value and hence verified successfully.

Student Signature :

S.P Ashwath

(Name : Ashwath Suresh Babu Piriya)