

Exp no:3	Realization of half-adder and full-adder logic circuits
Date: 23-09-2021	

Aim:

To realize the half-adder and full-adder logic circuits and verify the simulation output with theoretical results.

Required tools:

Multisim online circuit simulator

Theory:


Half-Adder:

A combinational logic circuit that performs the addition of two data bits, A and B, is called a half-adder. The addition will result in two output bits; one of which is the sum bit, S, and the other is the carry bit, C_{in} . The Boolean functions describing the half-adder are:

$$S = A \oplus B$$

$$C_{in} = AB$$

Logic Diagram:

 


Full-Adder:

A combinational logic circuit that adds three data bits, A, B, and C is called a full-adder. The Boolean functions describing the full-adder are:

$$S = A \oplus B \oplus C$$

$$C_{in} = C(A \oplus B) + AB$$

Logic Diagram:

 

Results:

Comparison of theoretical results with simulation results for Half Adder

A	B	Theoretical result according to the expression		Simulation result	
		SUM	CARRY	SUM	CARRY
0	0	0	0	0	0
0	1	1	0	1	0
1	0	1	0	1	0
1	1	0	1	0	1

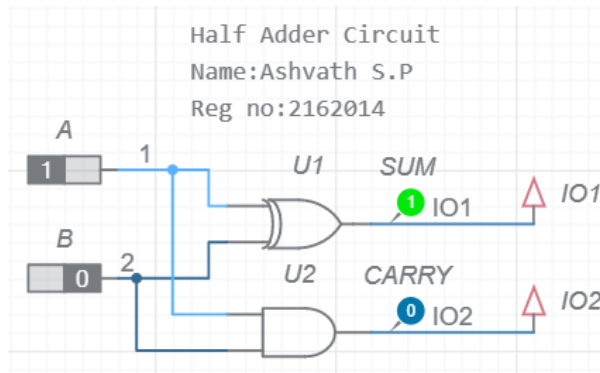


Figure: Logic circuit realization of Half-adder

Comparison of theoretical results with simulation results for Full Adder

A	B	C	Theoretical result according to the expression		Simulation result	
			SUM	CARRY	SUM	CARRY
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	1	0	1	0
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	1	0	1
1	1	0	0	1	0	1
1	1	1	1	1	1	1

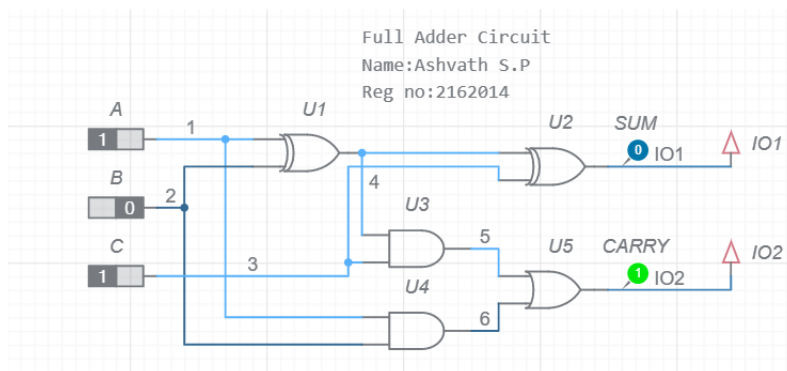


Figure: Logic circuit realization of full-adder

Inference:

The theoretical and simulation results of the truth table of half-adder and full-adder are in good agreement and verified successfully through multisim online simulator.

Student signature:

S.P. Ashvath

Marks:

Faculty signature: